

IC Design

Homework # 4


(Due 2021/12/30, 9:00, Verilog code and report upload to CEIBA, no hardcopy)

✧ Plagiarism is not allowed. 10% penalty for each day of delay.

Problem Specification

Design a divider circuit with reset that computes the **quotient Q and remainder R of two numbers A and B**. There are three input signals for the circuit, i.e., i_a with 8 bits, i_b with 5 bits and a 1-bit i_in_valid. The circuit contains three output signals, i.e., 8-bit o_q for the quotient, 5-bit o_r for the remainder and a 1-bit o_out_valid. Note that all the input and the output signals are **unsigned integers**. The divisor B is guaranteed to be **non-zero**. The relation between the input and the output signals is

$$A = Q * B + R.$$

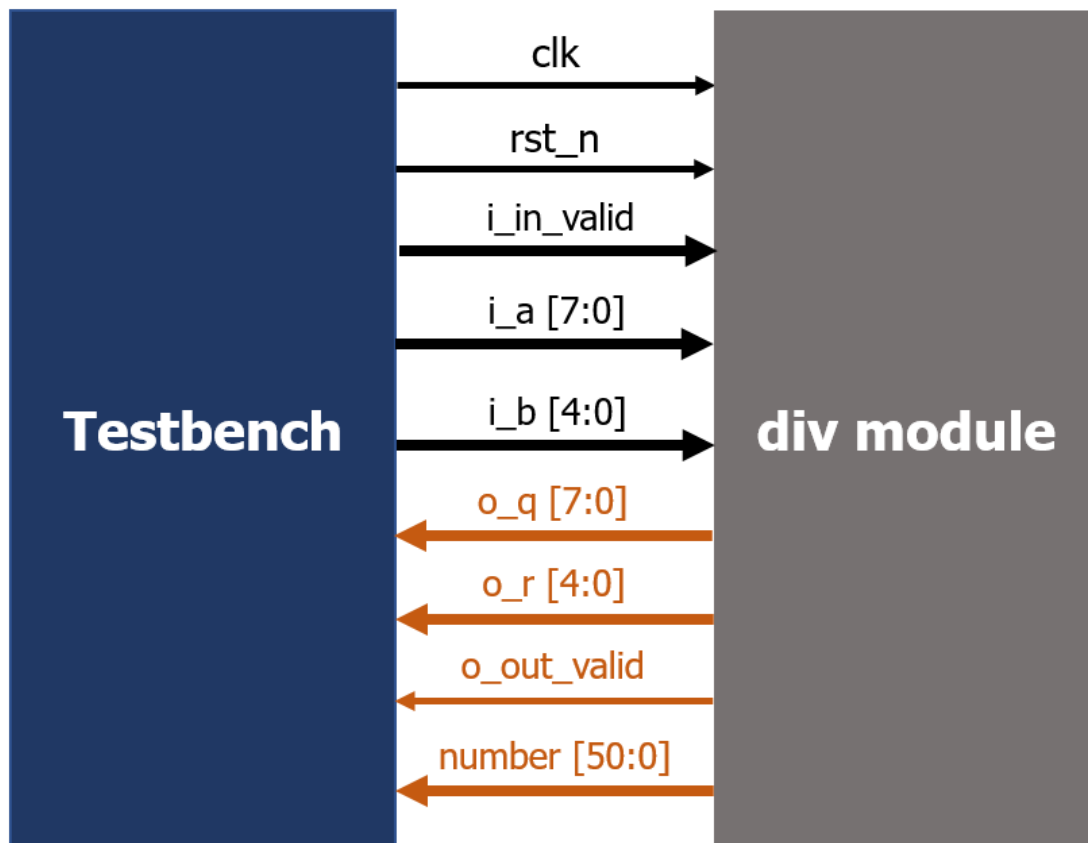


Pull up “o_out_valid” and output your answer to “o_q[7:0]” and “o_r[4:0]” once your circuit finish the calculation, the testbench will then check your answers. Note that the output signals: “o_q [7:0]” , “o_r[4:0]” and “o_out_valid” must be registered, i.e., they are outputs of DFFs **(use module FD2 (positive edge) in lib.v)**.

Timing Diagram

Since a design can be either recursive or pipelined, the testbench provides two input strategies, i.e., recursive and pipeline.

 
1. Recursive

In the recursive input strategy, **the circuit would be reset before every new input.**



 2. Pipeline

In the pipeline input strategy, the circuit would only be reset once. After reset, **new values of i_a and i_b would be input at every cycle.** Besides, **o_out_valid** should **maintain high once it was pulled up**, and the order of input a and b and their corresponding quotient and remainder should not be changed (**First in, first out.**).



Signals Description

Signal name	I/O	Width	Simple description
clk	Input	1	Clock signal.
rst_n	Input	1	Active low asynchronous reset.
i_in_valid	Input	1	Indicate that the input is valid
i_a	Input	8	Dividend
i_b	Input	5	Divisor
o_q	Output	8	Quotient
o_r	Output	5	Remainder
o_out_valid	Output	1	Indicate that the calculation was finished.
number	Output	51	The number of transistors.

Design Rules

Those who do not design according to the following rules will not be graded.

- **LUT-based designs are not allowed.**
- There should be a **reset signal** for the register.
- You are free to add pipeline registers.
- You can loosen your simulation timing first, (i.e., ``define CYCLE XXXX` in the tb.v), then shorten the clock period to find your critical path.
- Your design should be based on the **standard cells in the lib.v**. All logic operations in your design **MUST consist of the standard cells** instead of using the operands such as “+”, “-”, “&”, “|”, “>”, and “<”.
- Using “assign” to concatenate signals or specify constant values is allowed.
- Design your homework in the given “div.v” file. **You are NOT ALLOWED to change the filename and the header of the top module (i.e. the module name and the I/O ports).**
- If your design contains more than one module, **don’t create a new file for them**, just put those modules in “div.v.”

Grading Policy

1. Gate-level design using Verilog (70%)

Your score will depend on both the correctness and performance of your design.

(a) Correctness Score (40%)

At this stage, we will only evaluate whether the function of the divider module is correct. Time and area are not considered. We provide a testbench with 1000 patterns, which automatically grades your design. Your score in this part will be

$$40 \times \frac{\text{correct number}}{1000}.$$

(b) Performance Score (30%)

At this stage, you need to **add up the number of transistors of all used cells in the div module and connect it to number [50:0]**.

Only in this section, you are allowed to use “+” to help with calculations.

```
14 assign number = gate_count[0] + gate_count[1] + gate_count[2] + gate_count[3];
15
16 DRIVER V1 (.A(pp1_w[9]), .Z(pp1_w[10]), .number(gate_count[0]));
17 DRIVER V2 (.A(pp1_w[9]), .Z(pp1_w[11]), .number(gate_count[1]));
18 DRIVER V3 (.A(pp1_w[9]), .Z(pp1_w[12]), .number(gate_count[2]));
19 DRIVER V4 (.A(pp1_w[9]), .Z(pp1_w[13]), .number(gate_count[3]));
```

We will rank all students who pass (a) and have **no connection errors on number [50:0] port**. There will be a ranking according to **A*T**, where A represents the **number of transistors** and T represents the **total execution time**. Your performance score will be graded by your ranking according to the table below.

Percentage of passing students	Performance Score
If your ranking > 90 %	30
80% ~ 90%	27
70% ~ 80%	24
60% ~ 70%	21
50% ~ 60%	18
40% ~ 50%	15
30% ~ 40%	12
20% ~ 30%	9
10% ~ 20%	6
0% ~ 10%	3
Using operands, not standard cell logic	0
Incorrect number [50:0] connection	0
Correctness failed	0
Plagiarism	0

2. Report (30%)

(a) Simulation (0%)

Specify your **minimum cycle time** and **which strategy you used**. **If you do not provide this information, You will not get any score for part 1(70%)**. **This minimum cycle time would be verified by TAs**. Also, please put the screenshot of the summary

provided by the testbench in the report.

(b) Circuit diagram (10%)

You are encouraged to use software to draw the architecture **instead of hand drawing**. Plot it **hierarchically** so that readers can understand your design easily. **All of the above will improve your report score.**

(5%) Plot the gate-level circuit diagram of your design.

(5%) Plot critical path on the diagram above.

(c) Discussion (20%)

Discuss your design.

- (3%) Introduce your design.
- (2%) How do you cut your pipelined or recursive design?
- (5%) How do you improve your critical path and the number of transistors?
- (5%) How do you trade-off between area and speed?
- (5%) Compare with other architectures you have designed (if any).

Notification

Following are the files you will need (available on the class website)

HW4.zip includes

■ **HW4_2021.pdf:** This document.

■ **HW4_tutorial_2021.pdf:** Tutorial in class.

■ **div.v:**

Dummy design file. Program the design in this file.

The header of the top module and the declaration of the I/O ports are predefined in this file and you are not allowed to change them.

■ **lib.v:** Standard cells.

■ **tb.v:**

The testbench for your design.

■ **pattern/Ina.dat & Inb.dat :**

Input patterns for the testbench. Please keep the hierarchy when simulation.

■ **pattern/Golq.dat & Golr:**


Patterns of the correct answers for the testbench. Please keep the hierarchy when simulation.

Submission

All students who do not submit files according to the rules **will get a 20% penalty.**

- You should upload a **zip file** to **CEIBA**, the file name is “HW4_Student ID”, e.g., HW4_b08901001.zip

 - Your file must conform to the following structure.



- Specify your cycle time and which input mode you prefer in CYCLE.txt, **all letters are in uppercase**, e.g.,

CYCLE - Notepad

```
File Edit Format View Help
5.0
PIPELINE|
```

CYCLE - Notepad

```
File Edit Format View Help
10.0
RECURSIVE|
```

Testbench

1. Description

- The output waveform will be dumped to file “div.fsd”, you can use nWave to examine it.
- You can change the number of test data to debug, but the final score will still test 1000 data. (**define PATTERN 1000**)
- You can enable the debug function, which will display the data sent and received.

```

Pattern 970 passed. / Input A: 30 / Input B: 17 / Output Q: 1 / Output R: 13 / Golden Q: 1 / Golden R: 13
Pattern 971 failed. / Input A: 117 / Input B: 15 / Output Q: X / Output R: x / Golden Q: 7 / Golden R: 12
Pattern 972 passed. / Input A: 240 / Input B: 24 / Output Q: 10 / Output R: 0 / Golden Q: 10 / Golden R: 0
Pattern 973 passed. / Input A: 144 / Input B: 23 / Output Q: 6 / Output R: 6 / Golden Q: 6 / Golden R: 6
Pattern 974 passed. / Input A: 228 / Input B: 24 / Output Q: 9 / Output R: 12 / Golden Q: 9 / Golden R: 12
Pattern 975 passed. / Input A: 200 / Input B: 9 / Output Q: 22 / Output R: 2 / Golden Q: 22 / Golden R: 2
Pattern 976 failed. / Input A: 227 / Input B: 7 / Output Q: X / Output R: x / Golden Q: 32 / Golden R: 3
Pattern 977 passed. / Input A: 39 / Input B: 6 / Output Q: 6 / Output R: 3 / Golden Q: 6 / Golden R: 3
Pattern 978 passed. / Input A: 189 / Input B: 30 / Output Q: 6 / Output R: 9 / Golden Q: 6 / Golden R: 9
Pattern 979 failed. / Input A: 0 / Input B: 1 / Output Q: X / Output R: x / Golden Q: 0 / Golden R: 0
Pattern 980 failed. / Input A: 107 / Input B: 13 / Output Q: X / Output R: x / Golden Q: 8 / Golden R: 3
Pattern 981 passed. / Input A: 95 / Input B: 27 / Output Q: 3 / Output R: 14 / Golden Q: 3 / Golden R: 14
Pattern 982 passed. / Input A: 104 / Input B: 22 / Output Q: 4 / Output R: 16 / Golden Q: 4 / Golden R: 16
Pattern 983 passed. / Input A: 193 / Input B: 30 / Output Q: 6 / Output R: 13 / Golden Q: 6 / Golden R: 13
Pattern 984 passed. / Input A: 78 / Input B: 8 / Output Q: 9 / Output R: 6 / Golden Q: 9 / Golden R: 6
  
```

- If you pass the simulation, you should see:

```

=====
Simulation passed
=====
  
```

Otherwise, you would see:

```
=====
Simulation failed
=====
```

You would also see the summary:

```
=====
Summary
=====
Clock cycle:          3.7 ns
Number of transistors: 4201
Total excution cycle: 1007
Correctness Score:    40.0
Performance Score:    15652505.9
=====
```

Note that the performance score is the A*T value that would be used in ranking.

2. *Simulation command*

(a) *Recursive*

```
> ncverilog tb.v div.v lib.v +access+r
> ncverilog tb.v div.v lib.v +access+r +define+DEBUG
```

(b) *Pipeline*

```
> ncverilog tb.v div.v lib.v +access+r +define+PIPELINE
> ncverilog tb.v div.v lib.v +access+r +define+DEBUG+PIPELINE
```

TA email: r09943022@ntu.edu.tw, EE2-329

HW4 Office hours: (Mon) 13:00~16:00 @EE2-329

(Wed) 13:00~16:00 @EE2-329

If you are not convinient during office hours, you can email TA to make an alternative appointment.